

# **Meta-Programming**

**Pat Hanrahan**

**CS448H: Agile Hardware Design  
Winter 2017**

# Magma Product Types


$T = \text{Bit} \mid \text{Array}(n, T) \mid \text{Tuple}(T_1, T_2, \dots, T_n)$

- **Recursive product type (not algebraic data type)**
- **All types have fixed size**

$\text{Array}(n, T)$


$\text{Tuple}(T_1, T_2, \dots, T_n)$

 - **Calling these functions returns a type (class)**
- **Generalizes *higher-kinded* types**


 
# Mantle

**Standard Low-Level Hardware Library  
(think libc and libm, TTL 7400 / CMOS 4000)**



## **Mantle libc for hardware**

**And, Or, Xor, ...  
Add, Sub, ...  
Mux,  
Registers  
Shift registers  
Counters  
Memories  
...**

**see `mantle.md`**

# Higher-Order Circuits



# Instantiate Circuits

```
lut4 = LUT4(I0&I1)  
dff = DFF()
```

**Circuits are "like" functions**



**Use higher-order operators to  
constructor new circuits from other  
circuits**

# FullAdder - fulladder/fulladder.py

  

fork


**Invert(n)**

  



**join**




Add(n) - add/{add1,add2}.py

 

**fold**

  

**scan**

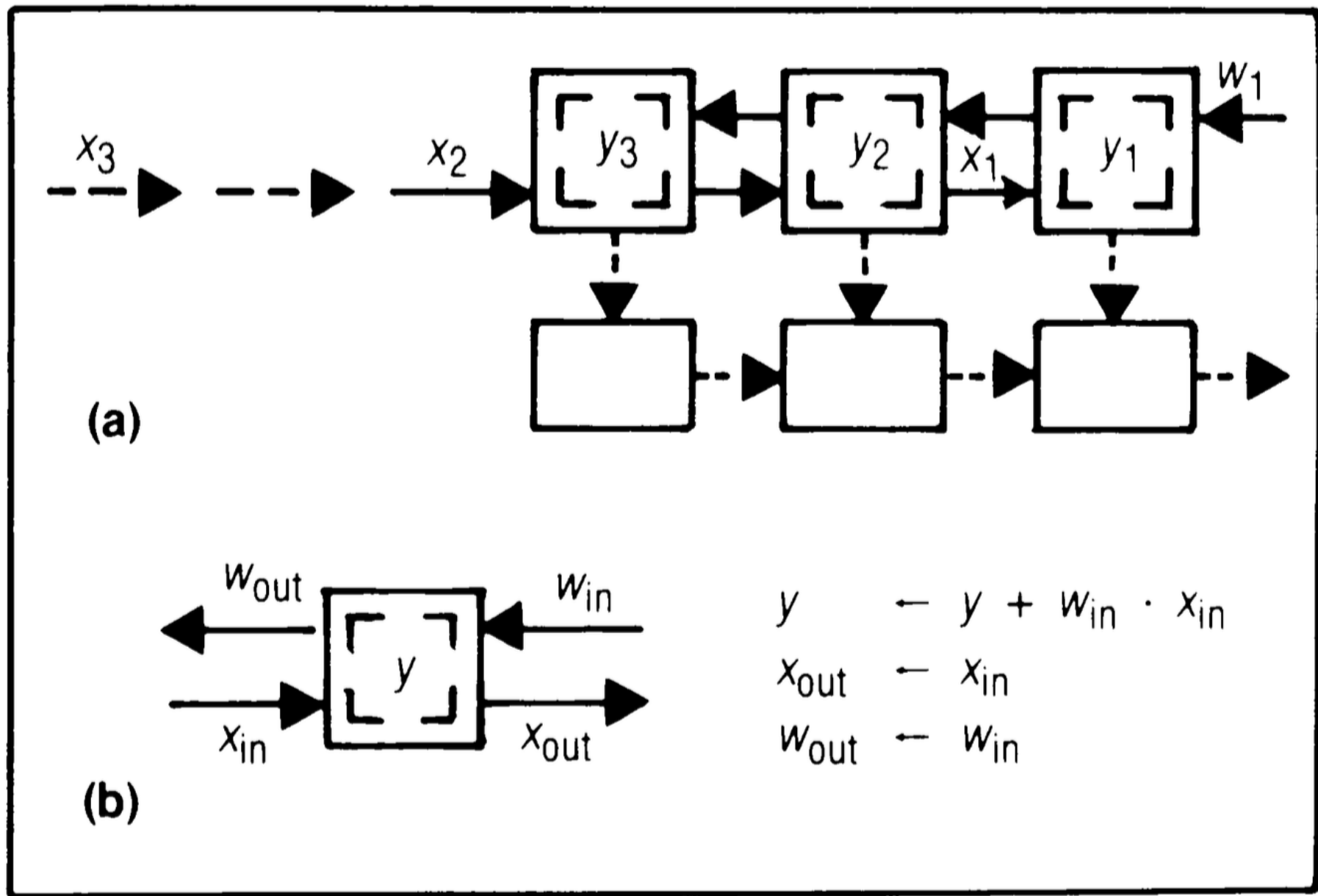

**Figure 6. Design R1: systolic convolution array (a) and cell (b) where  $y_i$ 's stay and  $x_i$ 's and  $y_i$ 's move in opposite directions systolically.**

**# Beyond functional programming ...**

**# Higher-order circuits**

```
def braid(circuits,  
    joinargs=[],  
    flatargs=[],  
    forkargs=[],  
    foldargs={}, rfoldargs={},  
    scanargs={}, rscanargs={}):
```

**...**

**# easily generalized to 2D**

```
// uncurry and curry
```

```
LUT2 = DeclareCircuit('LUT2',  
    "I0", In(Bit), "I1", In(Bit),  
    "O", Out(Bit))
```

```
lut1 = LUT2()  
assert str(lut1.interface) ==  
    'I0 : In(Bit), I1 : In(Bit) -> O : Out(Bit)'
```

```
lut2 = uncurry(lut1)  
assert str(lut2.interface) ==  
    'I : Array(2,In(Bit)) -> O : Out(Bit)'
```

```
lut3 = curry(lut2)  
assert str(lut3.interface) ==  
    'I0 : In(Bit), I1 : In(Bit) -> O : Out(Bit)'
```

```
// curry and uncurl
```

```
ROM2 = DeclareCircuit('ROM2',  
    "I", In(Array(2,Bit)),  
    "O", Out(Bit))
```

```
rom1 = ROM2()  
assert str(rom1.interface) ==  
    'I : Array(2,In(Bit)) -> O : Out(Bit)'
```

```
rom2 = curry(rom1)  
assert str(rom2.interface) ==  
    'I0 : In(Bit), I1 : In(Bit) -> O : Out(Bit)'
```

```
rom3 = uncurry(rom2)  
assert str(rom3.interface) ==  
    'I : Array(2,In(Bit)) -> O : Out(Bit)'
```

# **Circuit Definitions**

## **(Modules)**

# Circuit Definition

## 1. Generate Circuit class (new type)

```
Register2 = DefineRegister(2)
```

## 2. Instance Circuit

```
register2 = Register2()
```

## 3. Wire circuit instances

```
0 = register2(I)
```



```
def DefineRegister(n):  
    reg = DefineCircuit('Register'+str(n),  
                        "I", In(Array(n,Bit)),  
                        "O", In(Array(n,Bit)),  
                        "CLK", In(Bit))  
  
    ffs = join(col(FF, n))  
    wire(ffs(reg.I), reg.O)  
    wire(reg.CLK, ffs.CLK)  
  
    EndCircuit()  
    return reg  
  
Register2 = DefineRegister(2)  
register = Register2()  
wire(register(I), 0)
```

```
def DefineRegister(n):  
  
    T = In(Array(n, Bit))  
    class _Register(Circuit):  
        name = 'Register'+str(n)  
        IO = ["I",T,  
              "O",T,  
              "CLK", In(Bit)]  
  
        @classmethod  
        def definition(reg):  
            ffs = join(FFs(n))  
            wire(ffs(reg.I), reg.O)  
            wire(reg.CLK, ffs.CLK)  
  
    return _Register
```

```

def DefineSISO(n):
    """
        Generate Serial-In, Serial-Out shift register.

        I : Bit -> O : Bit
    """
    class _SISO(Circuit):
        name = 'SISO'+str(n)
        IO = ['input I',Bit, 'output O',Bit]+ClockInterface()

        @classmethod
        def definition(sono):
            ffs = FFs(n)
            reg = braid(ffs, foldargs={"I":"O"})
            reg(sono.I)
            wire(reg.0, sono.0)
            wireclock(sono, reg)

    return _SISO

```

```

def DefineSIP0(n):
    """
        Generate Serial-In, Parallel-Out shift register.

        I : Bit -> 0 : Array(n, Bit)
    """
    T = Array(n, Bit)
    class _SIP0(Circuit):
        name = 'SIP0'+str(n)
        IO = ['input I',Bit,'output 0',T]+ClockInterface()


        @classmethod
        def definition(sipo):
            ffs = FFs(n)
            reg = braid(ffs, scanargs={"I":"0"})
            wire(sipo.I, reg.I)
            wire(reg.0, sipo.0)
            wireclock(sipo, reg)

    return _SIP0

```
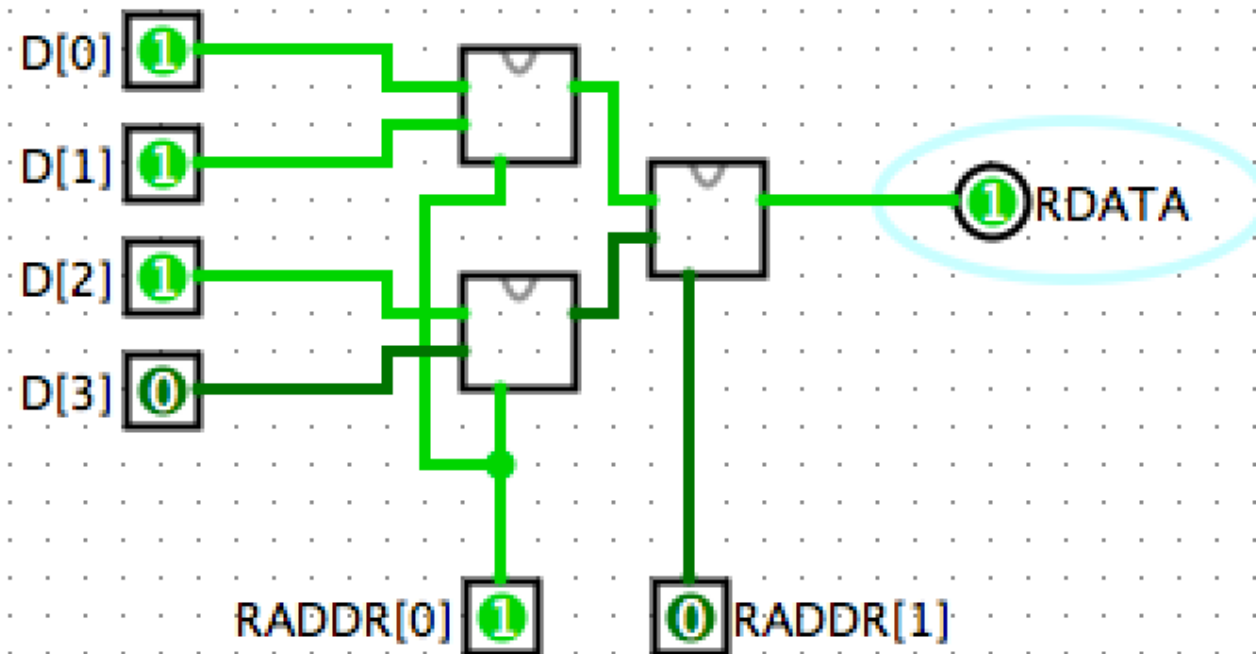
# **ROM and RAM**


ROM(2) :: RADDR:Array(4,Bit) -> RDATA:Bit



```

RAM(2) :: RADDR:Array(4,Bit),
         WDATA:Bit, WADDR:Array(4,Bit), WE:Bit
-> RDATA:Bit

```

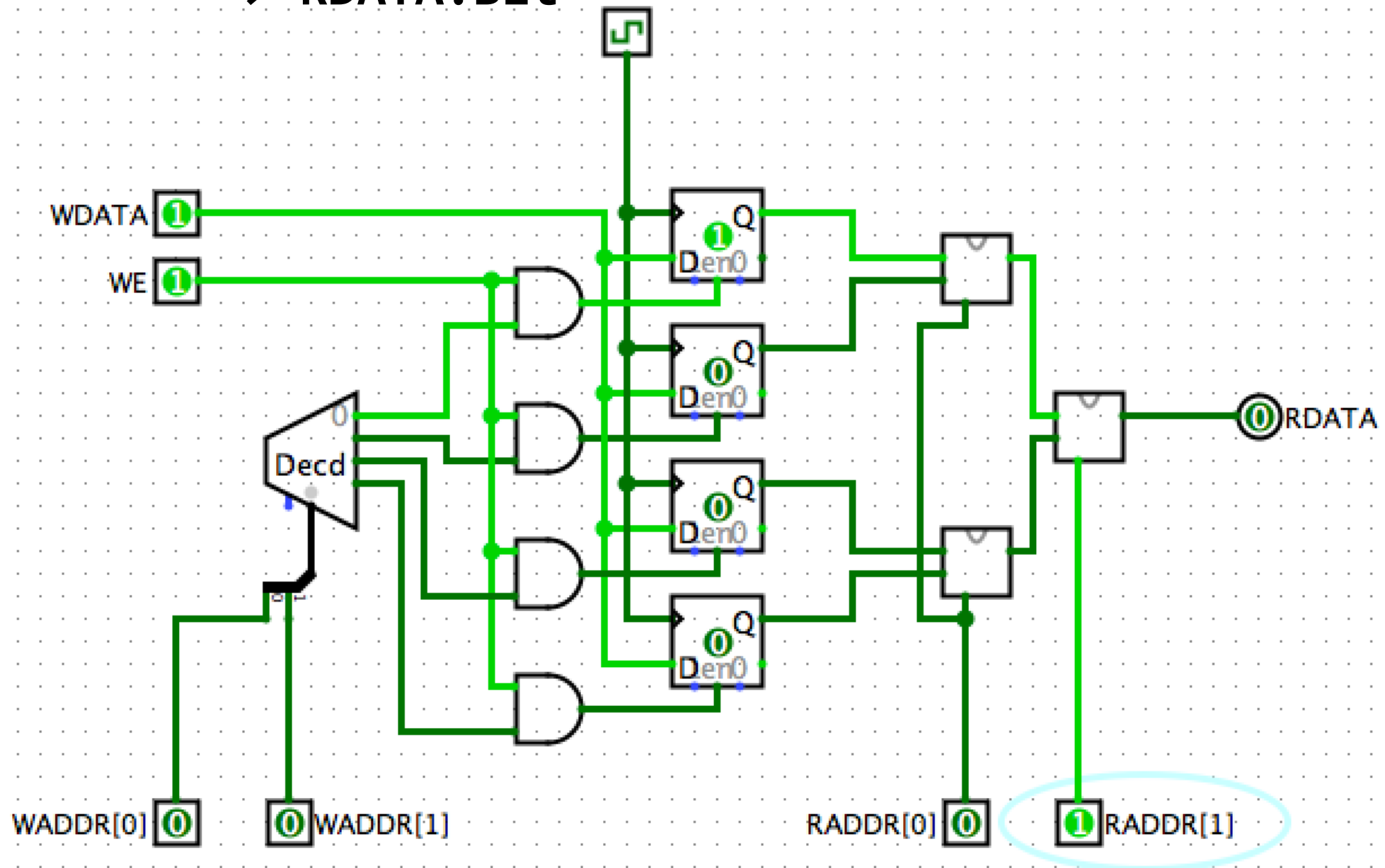


**UART**


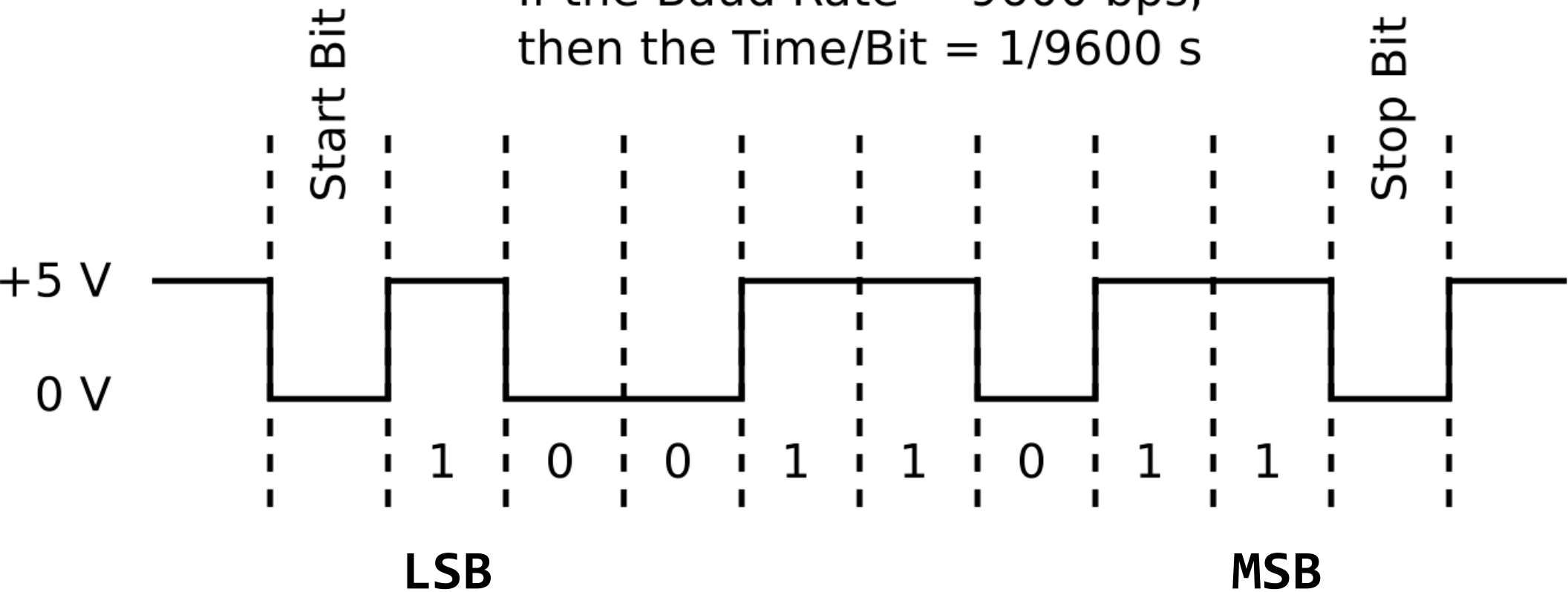
# Serial Protocol

If the Baud Rate = 9600 bps,  
then the Time/Bit =  $1/9600$  s



```
void bit(int val)
{
    gpio_write(pin, val);
    delay_us(DELAY);
}

void putc(int c)
{
    bit(0); // start bit
    // output 8-bits, lsb first
    for ( int i = 0; i < 8; i++ ) {
        bit(c & 0x1);
        c >>= 1;
    }
    bit(1); // 2 stop bits
    bit(1);
}
```

# fsm.py

RVD R'

000 0

001 0

010 1


011 0

100 1


101 0

110 1


111 0

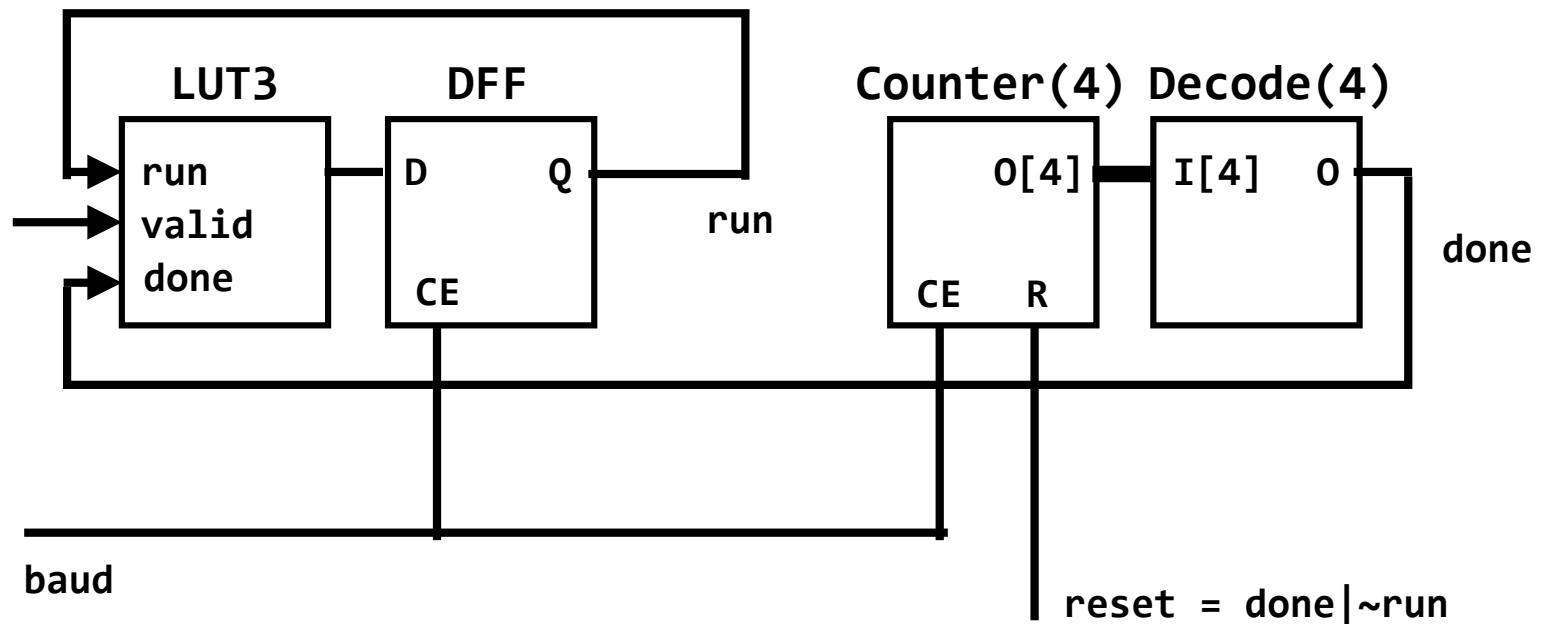


# baud.py

 

# fsm.py

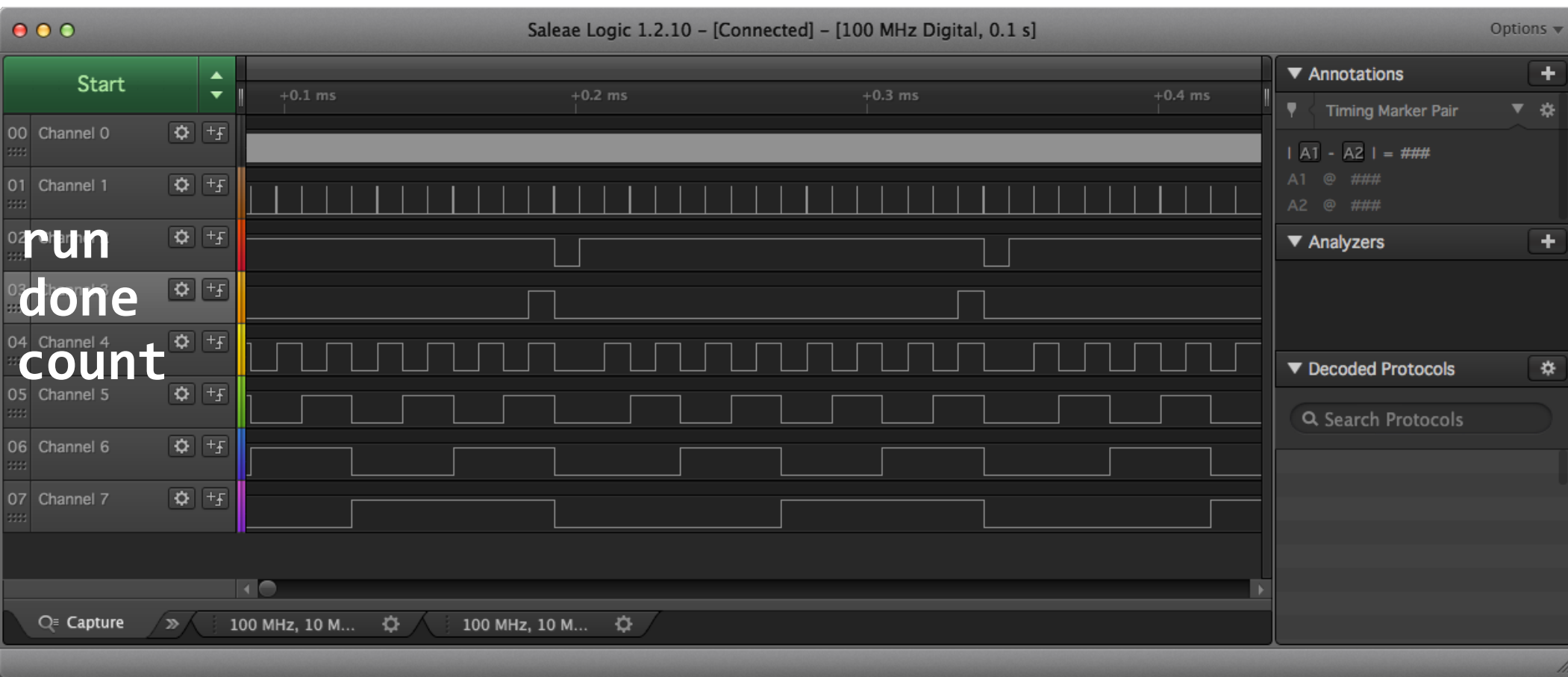


# uart.py

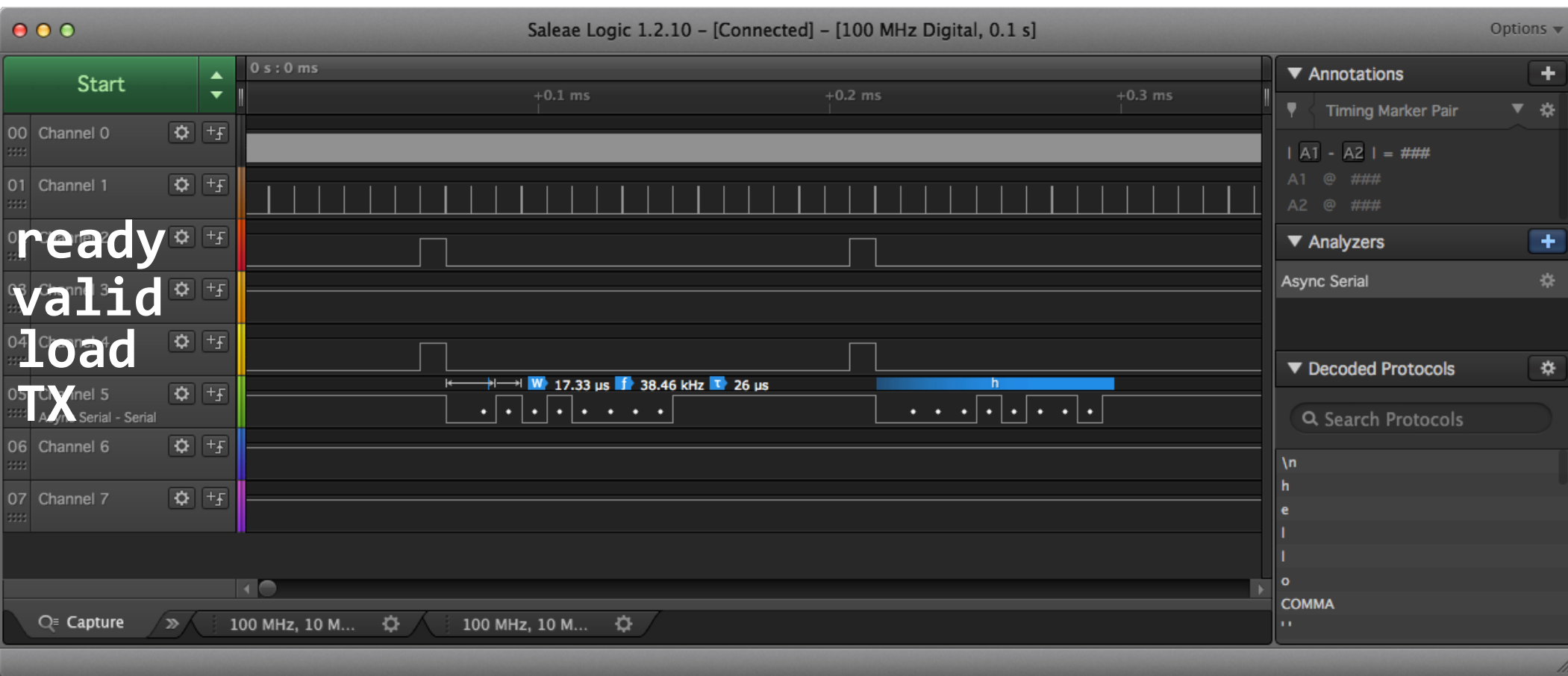

**LFSR**

# Linear Feedback Shift Register

 

0001  
1000  
0100  
0010  
1001  
1100  
0110  
1011  
0101  
1010  
1101  
1110  
1111  
0111  
0011  
0001



## **BITS, TAPS**

**3, "3, 2"**

**4, "4, 3"**

**5, "5, 3"**

**6, "6, 5"**

**7, "7, 6"**

**8, "8, 6, 5, 4"**

**9, "9, 5"**

**10, "10, 7"**

**11, "11, 9"**

**12, "12, 6, 4, 1"**

**13, "13, 4, 3, 1"**

**14, "14, 5, 3, 1"**

**15, "15, 14"**

**16, "16, 15, 13, 4"**

**17, "17, 14"**

**18, "18, 11"**

**19, "19, 6, 2, 1"**

**20, "20, 17"**

**21, "21, 19"**

**22, "22, 21"**

**23, "23, 18"**

**24, "24, 23, 22, 17"**

**25, "25, 22"**

**26, "26, 6, 2, 1"**

**27, "27, 5, 2, 1"**

**28, "28, 25"**

**29, "29, 27"**

**30, "30, 6, 4, 1"**

**31, "31, 28"**

**32, "32, 22, 2, 1"**